

For the bridge network in Fig. 2.54, find R_{ab} and i .

Answer: $60\ \Omega$, 4 A .

Practice Problem 2.15


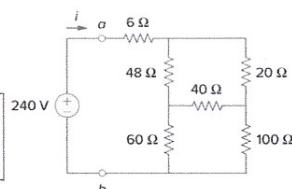
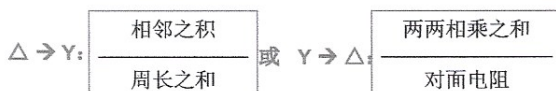


Figure 2.54
For Practice Prob. 2.15.

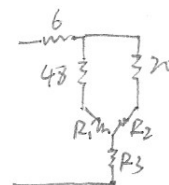

把右下降的 $40, 60, 100$ 叉换成 Y

$$R_1 = \frac{2400}{200} = 12; R_2 = \frac{4000}{200} = 20; R_3 = \frac{6000}{200} = 30$$

$$\therefore R_{ab} = 6 + (48 + 12) \parallel (20 + 20) + 30 = 36 + 60 \parallel 40 = 36 + 24 = 60\ \Omega$$

$$i = \frac{240}{60} = 4\text{ A}$$

44

Practice Problem 3.2

Find the voltages at the three nonreference nodes in the circuit of Fig. 3.6.

Answer: $v_1 = 32\text{ V}$, $v_2 = -25.6\text{ V}$, $v_3 = 62.4\text{ V}$.

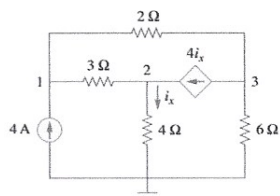


Figure 3.6
For Practice Prob. 3.2.

节点电压法, ②含受控电流源情况

$$\text{node 1: } 4 = \frac{v_1 - v_3}{2} + \frac{v_1 - v_2}{3}$$

$$\text{node 2: } \frac{v_1 - v_2}{3} + 4 \cdot \frac{v_3}{4} = \frac{v_2}{4}$$

$$\text{node 3: } \frac{v_1 - v_3}{2} = 4 \cdot \frac{v_2}{4} + \frac{v_3}{6}$$

$$\Rightarrow 5v_1 - 2v_2 - 3v_3 = 24$$

$$4v_1 + 5v_2 = 0$$

$$3v_1 - 6v_2 - 4v_3 = 0$$

$$\Rightarrow \begin{bmatrix} 5 & -2 & -3 \\ 4 & 5 & 0 \\ 3 & -6 & -4 \end{bmatrix} \cdot \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} 24 \\ 0 \\ 0 \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} 32 \\ -25.6 \\ 62.4 \end{bmatrix} \text{ V}$$

45

Find v_1 , v_2 , and v_3 in the circuit of Fig. 3.14 using nodal analysis.

Answer: $v_1 = 7.608 \text{ V}$, $v_2 = -17.39 \text{ V}$, $v_3 = 1.6305 \text{ V}$.

节点电压法, ④含受控电压源情况

把虚线框当作广义结点:

$$\begin{cases} \frac{v_1}{2} + \frac{v_2}{4} + \frac{v_3}{3} = 0 \\ v_1 - v_2 = 25 \\ -v_2 + v_3 = 5 \cdot \frac{v_1}{2} \end{cases}$$

$$\Rightarrow \begin{bmatrix} \frac{1}{2} & \frac{1}{4} & \frac{1}{3} \\ 1 & -1 & 0 \\ -\frac{5}{2} & -1 & 1 \end{bmatrix} \cdot \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 25 \\ 0 \end{bmatrix} \Rightarrow \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} 7.609 \\ -17.391 \\ 1.63 \end{bmatrix} \text{ V}$$

46

Practice Problem 3.4

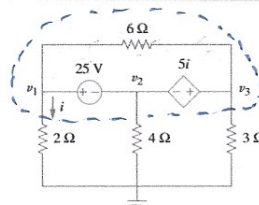


Figure 3.14
For Practice Prob. 3.4.

Practice Problem 3.6

Using mesh analysis, find I_o in the circuit of Fig. 3.21.

Answer: -4 A .

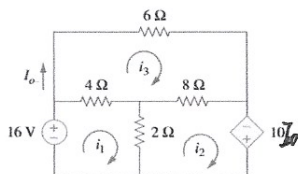


Figure 3.21
For Practice Prob. 3.6.

网孔电流法, ②含受控电压源情况

$$\text{loop 1: } -16 + (\dot{v}_1 - \dot{v}_3) \cdot 4 + (\dot{v}_1 - \dot{v}_2) \cdot 2 = 0$$

$$\text{loop 2: } (\dot{v}_2 - \dot{v}_1) \cdot 2 + (\dot{v}_2 - \dot{v}_3) \cdot 8 - 10\dot{v}_3 = 0$$

$$\text{loop 3: } (\dot{v}_3 - \dot{v}_1) \cdot 4 + \dot{v}_3 \cdot 6 + (\dot{v}_3 - \dot{v}_2) \cdot 8 = 0$$

$$\begin{aligned} 6\dot{v}_1 - 2\dot{v}_2 - 4\dot{v}_3 &= 16 \\ -2\dot{v}_1 + 10\dot{v}_2 - 18\dot{v}_3 &= 0 \\ -4\dot{v}_1 - 8\dot{v}_2 + 18\dot{v}_3 &= 0 \end{aligned} \Rightarrow \begin{bmatrix} \dot{v}_1 \\ \dot{v}_2 \\ \dot{v}_3 \end{bmatrix} = \begin{bmatrix} -2.571 \\ -7.714 \\ -4 \end{bmatrix} \text{ A}$$

47

Practice Problem 3.7

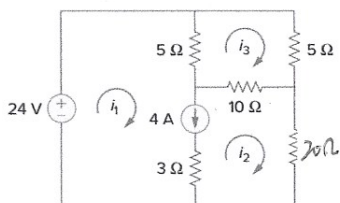
Use mesh analysis to determine i_1 , i_2 , and i_3 in Fig. 3.25.

Figure 3.25
For Practice Prob. 3.7.

$$i_1 = 4.8 \text{ A} \quad i_2 = 0.8 \text{ A} \quad i_3 = 1.6 \text{ A}$$

书上答案有错

网孔电流法, ③含电流源情况

去掉 4A branch, 把 loop 1 和 loop 2 看成广义网孔

$$-24 + (i_1 - i_3) \cdot 5 + (i_2 - i_3) \cdot 10 + i_2 \cdot 20 = 0$$

loop 3:

$$(i_3 - i_1) \cdot 5 + i_3 \cdot 5 + (i_3 - i_2) \cdot 10 = 0$$

另:

$$4 = i_1 - i_2$$

$$\begin{aligned} 48 \Rightarrow \quad & 5i_1 + 30i_2 - 15i_3 = 24 \\ & -5i_1 - 10i_2 + 20i_3 = 0 \\ & i_1 - i_2 = 4 \end{aligned}$$

$$\Rightarrow \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 4.8 \\ 0.8 \\ 1.6 \end{bmatrix} \text{ A}$$