

## Practice Problem 8.4

The circuit in Fig. 8.12 has reached steady state at  $t = 0^-$ . If the make-before-break switch moves to position  $b$  at  $t = 0$ , calculate  $i(t)$  for  $t > 0$ .

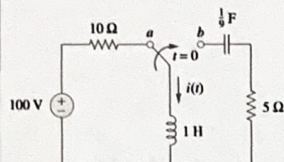


Figure 8.12  
For Practice Prob. 8.4.

Answer:  $e^{-2.5t}(10 \cos 1.6583t - 15.076 \sin 1.6583t)$  A.

串联RLC二阶电路的零输入响应

① 求初始值  $i(0) = 10$  A  $L \frac{di(0)}{dt} = -50 \Rightarrow \frac{di(0)}{dt} = -50$

②  $\alpha = \frac{R}{2L} = 2.5$ ,  $\omega_0 = \frac{1}{\sqrt{LC}} = 3$   $\alpha < \omega_0$  欠阻尼

$\therefore \omega_d = \sqrt{\omega_0^2 - \alpha^2} = 1.6583$

通解:  $e^{-\alpha t}(A_1 \cos \omega_d t + A_2 \sin \omega_d t)$

$i(0) = 10 \Rightarrow A_1 = 10$

$\frac{di(0)}{dt} = -50 \Rightarrow -\alpha A_1 + A_2 \omega_d = -50 \Rightarrow A_2 = -15.076$

56  $\therefore i(t) = e^{-2.5t}(10 \cos 1.6583t - 15.076 \sin 1.6583t)$  A

Refer to the circuit in Fig. 8.17. Find  $v(t)$  for  $t > 0$ .

Answer:  $50(e^{-10t} - e^{-2.5t})$  V.

## Practice Problem 8.6

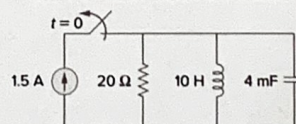


Figure 8.17

并联RLC二阶电路的零输入响应

① 初始值:  $v(0) = 0$

$C \frac{dv(0)}{dt} = -1.5$  ( $\because 20\Omega$  两端电压为 0, 电流不为 0)  $\Rightarrow \frac{dv(0)}{dt} = -37.5$

②  $\alpha = \frac{1}{2RC} = 6.25$   $\omega_0 = \frac{1}{\sqrt{LC}} = 5$   $\alpha > \omega_0$  过阻尼.  $s_1 = -2.5$   $s_2 = -10$

通解  $A_1 e^{-2.5t} + A_2 e^{-10t}$

代入初始值, 得到  $A_1 = -50$ ,  $A_2 = 50$

57  $\therefore v(t) = 50 e^{-10t} - 50 e^{-2.5t}$  V



## Practice Problem 8.7

Having been in position *a* for a long time, the switch in Fig. 8.21 is moved to position *b* at  $t = 0$ . Find  $v(t)$  and  $v_R(t)$  for  $t > 0$ .

串联RLC的阶跃响应 (全响应)

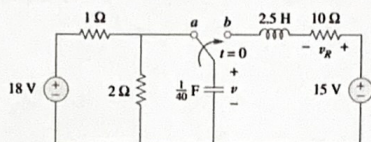


Figure 8.21  
For Practice Prob. 8.7.

Answer:  $15 - (1.7321 \sin 3.464t + 3 \cos 3.464t)e^{-2t}$  V,  
 $3.464e^{-2t} \sin 3.464t$  V.

$$\begin{cases} V(0) = 12 \\ C \frac{dV(0)}{dt} = 0 \Rightarrow \frac{dV(0)}{ds} = 0 \\ V(\infty) = 15 \end{cases}$$

$$\sigma = \frac{R}{2L} = 2 \quad \omega_0 = \frac{1}{\sqrt{LC}} = 4$$

$$\therefore \text{欠阻尼} \quad \omega_d = \sqrt{\omega_0^2 - \sigma^2} = 3.464$$

$$\text{通解: } 15 + e^{-2t} (A_1 \cos \omega_d t + A_2 \sin \omega_d t)$$

$$\text{代入初始值} \Rightarrow A_1 = -3; A_2 = 1.732$$

58

$$\therefore v(t) = 15 - e^{-2t} (3 \cos 3.464t + 1.732 \sin 3.464t) \text{ V}$$

$$\begin{aligned} i &= C \frac{dV}{dt}, \quad v_R = 10i = \frac{1}{C} \frac{dv}{dt} \\ &= 3.464 e^{-2t} \sin 3.464t \text{ V} \end{aligned}$$

Determine  $v$  and  $i$  for  $t > 0$  in the circuit of Fig. 8.28. (See comments about current sources in Practice Prob. 7.5.)

Answer:  $20(1 - e^{-5t})$  V,  $5(1 - e^{-5t})$  A.

## Practice Problem 8.9

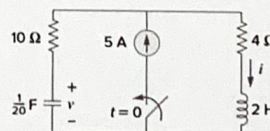


Figure 8.28  
For Practice Prob. 8.9.

$$\begin{cases} \text{① 初始值} \\ \text{② 稳态值} \end{cases} \begin{cases} V(0) = 0 \\ C \frac{dV(0)}{dt} = 5 \Rightarrow \frac{dV(0)}{ds} = 10 \\ V(\infty) = 20 \end{cases}$$

$$\text{② Turn off 独立源} \quad \begin{cases} -i = \frac{1}{20} \frac{dv}{dt} \\ -v + 14i + 2 \frac{di}{dt} = 0 \end{cases}$$

$$\text{③ 通解: } V(t) = 20 + A_1 e^{-2t} + A_2 e^{-5t}$$

$$\text{代入初始值} \Rightarrow A_1 = 20, A_2 = -20$$

$$\therefore v(t) = 20 - 20e^{-5t} \text{ V}$$

$$\Rightarrow \frac{d^2 v}{dt^2} + 7 \frac{dv}{dt} + 10 = 0 \Rightarrow \begin{cases} s_1 = -2 \\ s_2 = -5 \end{cases}$$

$$\begin{aligned} i(t) &= 5 - C \frac{dv}{dt} \\ &= 5 - 5e^{-5t} \text{ A} \end{aligned}$$