

Calculate the instantaneous power and average power absorbed by the passive linear network of Fig. 11.1 if

$$v(t) = 330 \cos(10t + 20^\circ) \text{ V} \quad \text{and} \quad i(t) = 33 \sin(10t + 60^\circ) \text{ A}$$

Answer: $3.5 + 5.445 \cos(20t - 10^\circ) \text{ kW}$, 3.5 kW .

Practice Problem 11.1

$$p(t) = v(t)i(t)$$

$$P = \frac{1}{T} \int_0^T p(t) dt$$

瞬时功率和平均功率的定义

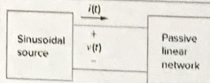


Figure 11.1
Sinusoidal source and passive linear circuit.

瞬时功率 $p(t) = v(t) \cdot i(t)$

$$= 330 \cos(10t + 20^\circ) \cdot 33 \sin(10t + 60^\circ)$$

$$= \left[\frac{1}{2} \sin(20t + 80^\circ) - \frac{1}{2} \sin(-40^\circ) \right] \cdot 330 \cdot 33$$

$$= 3500 + 5445 \cos(20t - 10^\circ) \text{ W}$$

平均功率为瞬时功率的常数项: 3.5 kW

Practice Problem 11.5

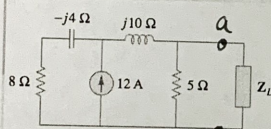


Figure 11.10
For Practice Prob. 11.5.

For the circuit shown in Fig. 11.10, find the load impedance Z_L that absorbs the maximum average power. Calculate that maximum average power.

Answer: $3.415 - j0.7317 \Omega$, 51.47 W .

共轭匹配

对 a-b 左边电路进行戴维南等效:

① 开路电压

$$V_{Th} = 12 \cdot \frac{(8 - j4)}{(8 - j4) + (5 + j10)} \cdot 5 = 23.415 - j29.268 \text{ V}$$

$$= 37.482 \angle -51.34^\circ$$

② 等效阻抗:

$$Z_{Th} = (8 + j6) \parallel 5 = 3.415 + j0.732 \Omega$$

$$\therefore Z_L = Z_{Th}^* = 3.415 - j0.732 \Omega$$

$$P_{max} = \frac{|V_{Th}|^2}{8 R_{Th}} = \frac{37.482^2}{8 \times 3.415} = 51.424 \text{ W}$$

Practice Problem 11.11

For a load, $V_{rms} = 110/85^\circ$ V, $I_{rms} = 3/15^\circ$ A. Determine: (a) the complex and apparent powers, (b) the real and reactive powers, and (c) the power factor and the load impedance.

从复功率导出其他所有功率量

Answer: (a) $330 \angle 70^\circ$ VA, 330 VA (b) 112.87 W, 310.1 VAR, (c) 0.342 lagging, $(12.541 + j34.46) \Omega$.

$$(a) \text{ 复功率 } \vec{S} = V_{rms} \cdot I_{rms}^* = 330 \angle 70^\circ = 112.867 + j310.099 \text{ VA}$$

视在功率为复功率的模: 330 VA

$$(b) \text{ 有功功率 (平均功率) 为复功率的实部: } 112.867 \text{ W}$$

无功功率为复功率的虚部: 310.099 VAR

$$(c) \text{ 功率因子 } pf = \frac{P}{S} = \frac{112.867}{330} = 0.342$$

$$Z = \frac{V_{rms}}{I_{rms}} = 12.541 + j34.455 \Omega$$

67

Find the value of parallel capacitance needed to correct a load of 140 kVAR at 0.85 lagging pf to unity pf. Assume that the load is supplied by a 220-V (rms), 60-Hz line.

Answer: 7.673 mF.

功率因数校正

Practice Problem 11.15

$$C = \frac{Q_c}{\omega V_{rms}^2} = \frac{P(\tan \theta_1 - \tan \theta_2)}{\omega V_{rms}^2}$$

$$Q = 140 \text{ kVAR}$$

$$C = \frac{Q}{\omega V_{rms}^2} = \frac{140 \text{ k}}{2\pi \cdot 60 \cdot 220^2} = 7.677 \text{ mF}$$

68