

Determine the phasor currents I_1 and I_2 in the circuit of Fig. 13.13.

Practice Problem 13.2


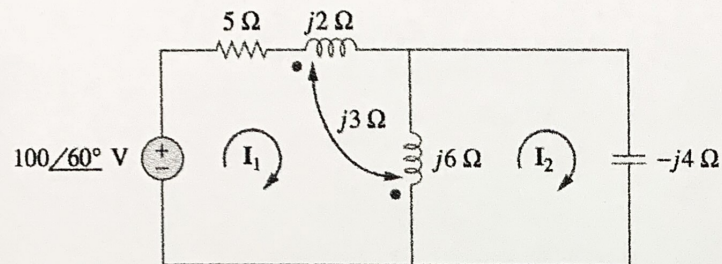


Figure 13.13
For Practice Prob. 13.2.

互感的概念~稍复杂情况
Focus on 流过线圈的电流

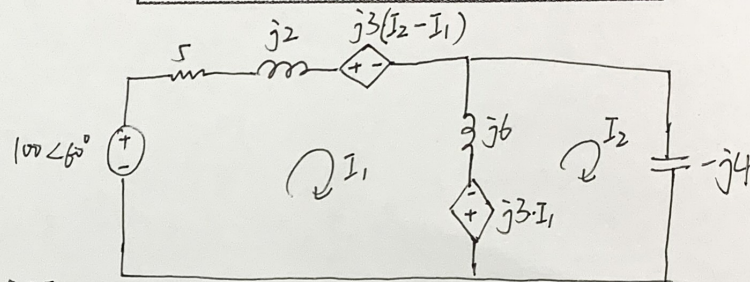

Answer: $I_1 = 17.889 \angle 86.57^\circ \text{ A}$, $I_2 = 26.83 \angle 86.57^\circ \text{ A}$.

$$-100 \angle 60^\circ + (5 + j2)I_1 - j6 \cdot I_2 + j3(I_2 - I_1) - j3I_1 = 0$$

$$j3I_1 + (I_2 - I_1) \cdot j6 - j4I_2 = 0$$

$$\Rightarrow \begin{bmatrix} 5 + j2 & -3j \\ -3j & j2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 100 \angle 60^\circ \\ 0 \end{bmatrix} \Rightarrow \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 17.889 \angle 86.565^\circ \\ 26.833 \angle 86.565^\circ \end{bmatrix} \text{ A}$$

For the circuit in Fig. 13.18, determine the coupling coefficient and the energy stored in the coupled inductors at $t = 1.5$ s.

Practice Problem 13.3

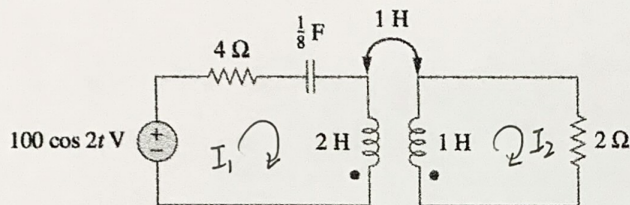


Figure 13.18
For Practice Prob. 13.3.

磁耦合系数和储能


$$k = \frac{M}{\sqrt{L_1 L_2}}$$

$$w = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 \pm M i_1 i_2$$

Answer: 0.7071, 246.2 J.

$$\textcircled{1} k = \frac{M}{\sqrt{L_1 L_2}} = \frac{1}{\sqrt{2}} = 0.707$$

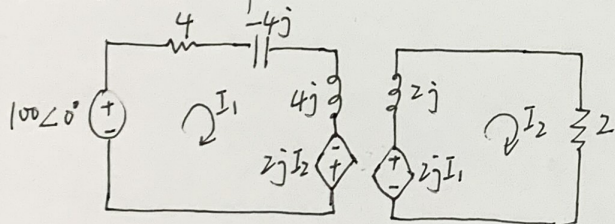② 频域分析, $\omega = 2$, $\frac{1}{8} F \Rightarrow -4j$, $2H \Rightarrow 4j$; $1H \Rightarrow 2j$



$$\Rightarrow \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 19.612 \angle 11.31^\circ \\ 13.868 \angle 56.31^\circ \end{bmatrix}$$

$$i_1(t) = 19.612 \cdot \cos(2t + 11.31^\circ)$$

$$i_2(t) = 13.868 \cdot \cos(2t + 56.31^\circ)$$

当 $t = 1.5$ s 时

$$W = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 - M i_1 i_2 = 245.099 \text{ J}$$


$$-100 \angle 0^\circ + 4I_1 - 2jI_2 = 0$$

$$-2jI_1 + (2 + 2j)I_2 = 0$$

$$\Rightarrow \begin{bmatrix} 4 & -2j \\ -2j & 2 + 2j \end{bmatrix} \cdot \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 100 \angle 0^\circ \\ 0 \end{bmatrix}$$

Find the input impedance of the circuit in Fig. 13.25 and the current from the voltage source.

Practice Problem 13.4

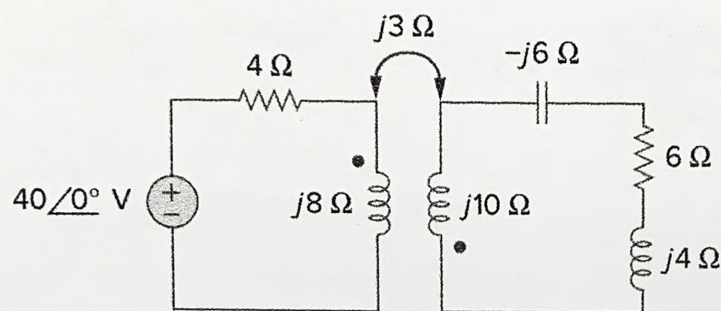

阻抗折算

$$\mathbf{Z}_R = \frac{\omega^2 M^2}{R_2 + j\omega L_2 + \mathbf{Z}_L}$$

Figure 13.25

For Practice Prob. 13.4.

Answer: $8.58 \angle 58.05^\circ \Omega$, $4.662 \angle -58.05^\circ \text{ A}$.

次级回路总阻抗: $6 + 8j$

ωM : $3j$

$$\Rightarrow \mathbf{Z}_{in} = 4 + 8j + \frac{3^2}{6 + 8j} = 8.58 \angle 58.05^\circ$$


$$\mathbf{I} = \frac{40 \angle 0^\circ}{\mathbf{Z}_{in}} = 4.662 \angle -58.05^\circ$$

Solve the problem in Example 13.1 (see Fig. 13.9) using the T-equivalent model for the magnetically coupled coils.


Practice Problem 13.6

Answer: $13 \angle -49.4^\circ$ A, $2.91 \angle 14.04^\circ$ A.

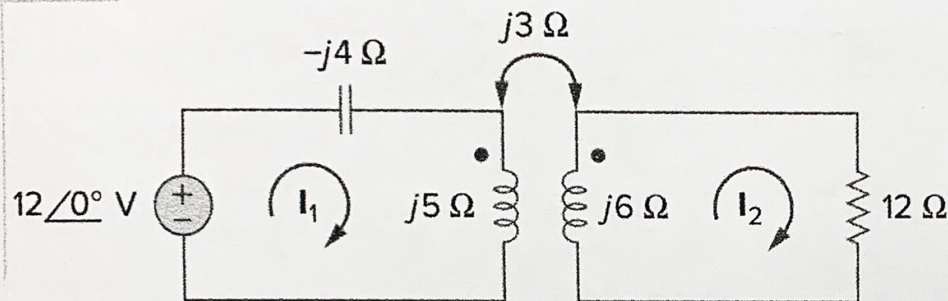Calculate the phasor currents I_1 and I_2 in the circuit



去耦合等效法

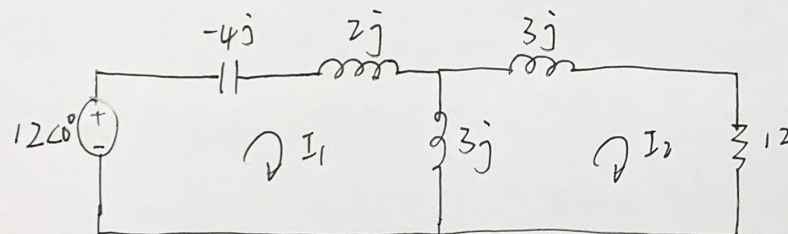

$$-12\angle 0^\circ + j1 \cdot I_1 - 3j I_2 = 0$$

$$(12 + 6j) I_2 - 3j I_1 = 0$$

$$\begin{bmatrix} j1 & -3j \\ -3j & 12+6j \end{bmatrix} \cdot \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 12\angle 0^\circ \\ 0 \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 13.016 \angle -49.39^\circ \\ 2.91 \angle 14.036^\circ \end{bmatrix} \text{ A}$$

In the ideal transformer circuit of Fig. 13.38, find V_o and the complex power supplied by the source.

Practice Problem 13.8

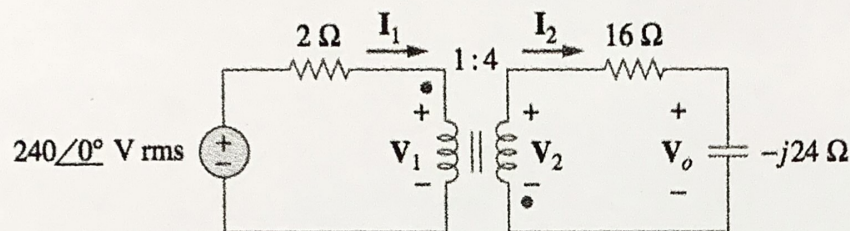


Figure 13.38
For Practice Prob. 13.8.

理想变压器的折算法简化

Answer: $429.4/116.57^\circ$ V, $17.174/-26.57^\circ$ kVA.

将 $16 - j24$ 折算到初级 $Z_{in} = \frac{16 - j24}{16} = 1 - j1.5$

$$\therefore I_1 = \frac{240}{3 - j1.5} = 71.554 \angle 26.565^\circ$$

$$I_2 = -\frac{1}{4} I_1$$

$$V_o = I_2 \cdot (-j24) = 429.325 \angle 116.565^\circ$$

$$P = V \cdot I^* = 240 \cdot 71.554 \angle -26.565^\circ = 1.717 \angle -26.565^\circ \times 10^4 \text{ VA}$$

Practice Problem 13.9

Find V_o in the circuit of Fig. 13.40.

折算法简化不能应用时，
采用传统电路分析法

$$\frac{V_1}{V_2} = \frac{1}{2}, \quad \frac{I_1 - I_3}{I_2 - I_3} = -\frac{2}{1}$$

$$-240 + 4I_1 + V_1 = 0$$

$$V_2 + 10I_2 - 2I_3 = 0$$

$$-V_1 + 8I_3 + 2(I_3 - I_2) - V_2 = 0$$

$$2V_1 - V_2 = 0$$

$$I_1 - I_3 + 2(I_2 - I_3) = 0$$

$$\begin{bmatrix} 1 & 0 & 4 & 0 & 0 \\ 0 & 1 & 0 & 10 & -2 \\ -1 & -1 & 0 & -2 & 10 \\ 2 & -1 & 0 & 0 & 0 \\ 0 & 0 & 1 & 2 & -3 \end{bmatrix} \cdot \begin{bmatrix} V_1 \\ V_2 \\ I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 240 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

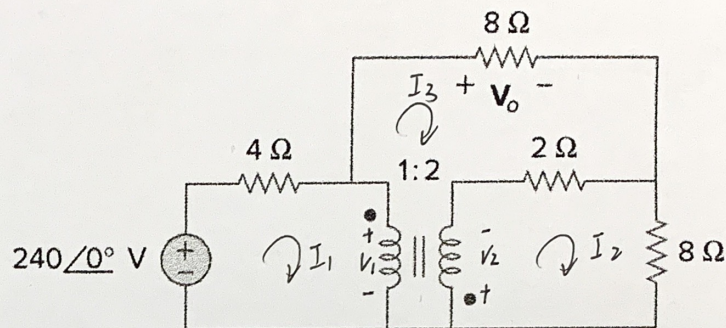


Figure 13.40
For Practice Prob. 13.9.

Answer: 96 V.

$$\Rightarrow \begin{bmatrix} V_1 \\ V_2 \\ I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 44.308 \\ 88.615 \\ 48.923 \\ -6.462 \\ 12 \end{bmatrix}$$

$$\therefore V_o = I_3 \cdot 8 = 96 \text{ V}$$