
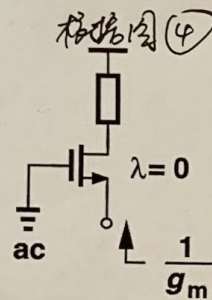
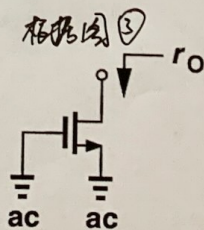
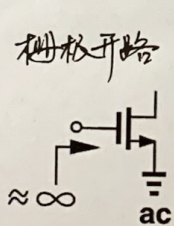
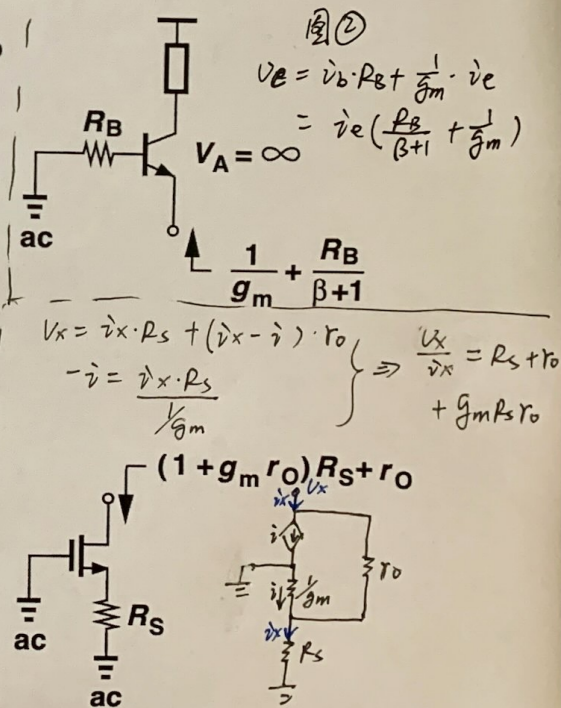
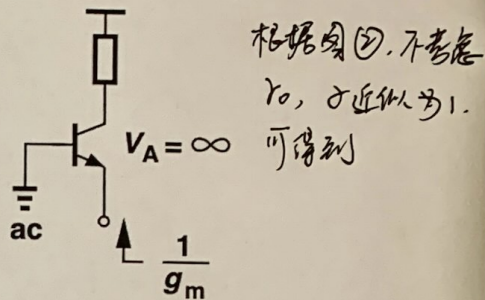
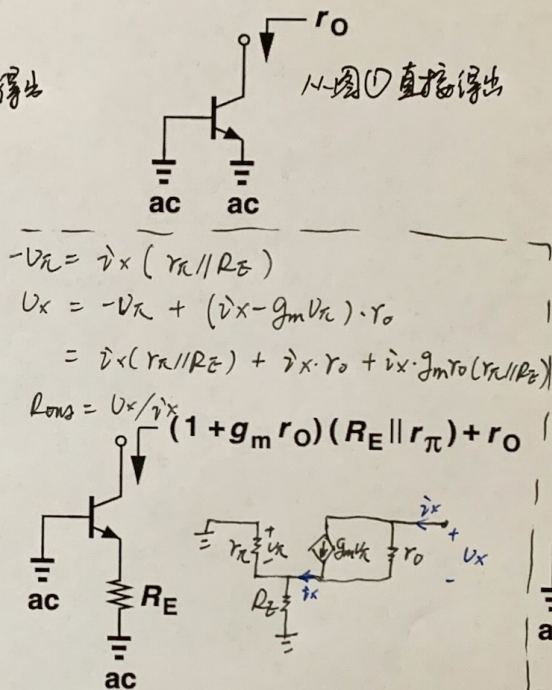
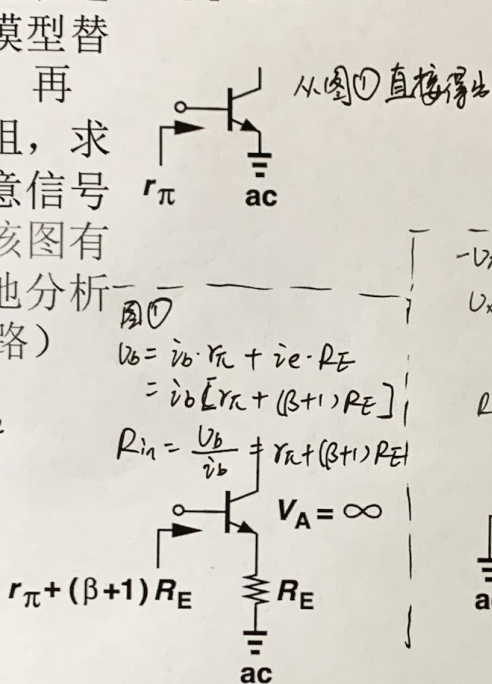


验证常见结构的小信号输入输出电阻表达式（用小信号模型替代MOSFET/BJT，再求输入输出电阻，求输出电阻时注意信号源短路。熟记该图有利于快速直观地分析MOSFET/BJT电路）

作业

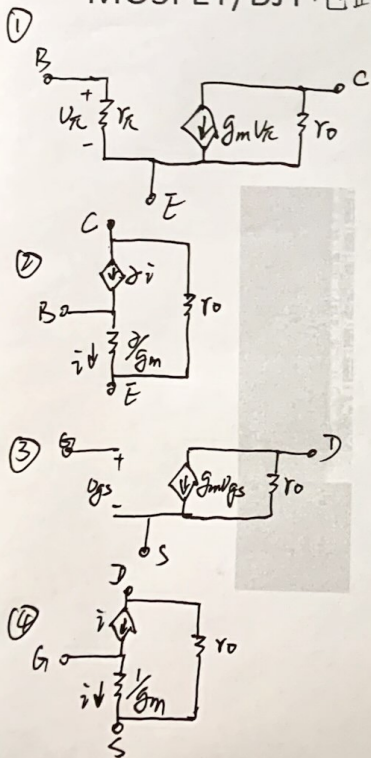

7.4 For the amplifier in Fig. 7.10, let $V_{DD} = 5\text{ V}$, $R_D = 10\text{ k}\Omega$, $V_t = 1\text{ V}$, $k'_n = 20\text{ }\mu\text{A/V}^2$, $W/L = 20$, $V_{GS} = 2\text{ V}$, and $\lambda = 0$.

(a) Find the dc current I_D and the dc voltage V_{DS} . $I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} V_{ov}^2 = 200\text{ }\mu\text{A}$ $V_{DS} = 5 - 10\text{ k} \cdot 0.2\text{ mA} = 3\text{ V}$

(b) Find g_m . $g_m = \frac{I_D}{V_{ov}/2} = \frac{0.2\text{ mA}}{0.5\text{ V}} = 0.4\text{ mA/V}$

(c) Find the voltage gain. $A_v = -g_m R_D = -4\text{ V/V}$


(d) If $v_{gs} = 0.2 \sin \omega t$ volts, find v_{ds} assuming that the small-signal approximation holds. What are the minimum and maximum values of v_{DS} ? $v_{ds} = v_{gs} \cdot A_v = -0.8 \sin \omega t\text{ V}$, $V_{DS} + 0.8 = 3.8\text{ V}$ $V_{DS} - 0.8\text{ V} = 2.2\text{ V}$

(e) Use Eq. (7.28) to determine the various components of i_D . Using the identity $\sin^2 \omega t = \frac{1}{2} - \frac{1}{2} \cos 2\omega t$, show that there is a slight shift in I_D (by how much?) and that there is a second-harmonic component (i.e., a component with frequency 2ω). Express the amplitude of the second-harmonic component as a percentage of the amplitude of the fundamental. (This value is known as the second-harmonic distortion.)

Ans. (a) 0.2 mA , 3 V ; (b) 0.4 mA/V ; (c) -4 V/V ; (d) $v_{ds} = -0.8 \sin \omega t$ volts, 2.2 V , 3.8 V ; (e) $i_D = (204 + 80 \sin \omega t - 4 \cos 2\omega t)\text{ }\mu\text{A}$, 5%


$$i_D = \frac{1}{2} k_n (V_{GS} + v_{gs} - V_t)^2$$
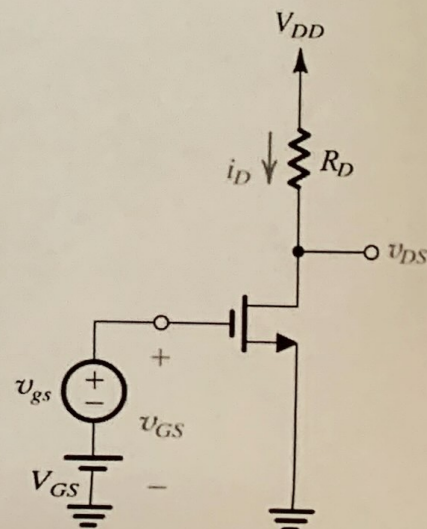
$$= \frac{1}{2} k_n (V_{GS} - V_t)^2 + k_n (V_{GS} - V_t) v_{gs} + \frac{1}{2} k_n v_{gs}^2 \quad (7.28)$$



D7.10 Consider the amplifier circuit of Fig. 7.16(a) without the load resistance R_L and with channel-length modulation neglected. Let $V_{DD} = 5$ V, $V_t = 0.7$ V, and $k_n = 1$ mA/V². Find V_{OV} , I_D , R_D , and R_G to obtain a voltage gain of -25 V/V and an input resistance of 0.5 M Ω . What is the maximum allowable input signal, $\hat{v}_i$?

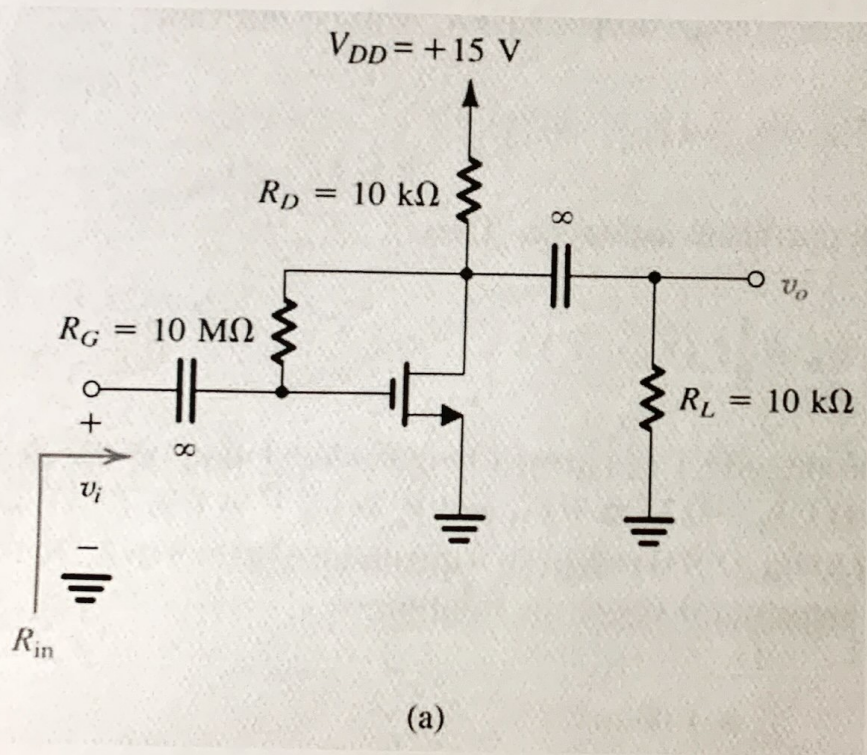Ans. 0.319 V; 50.9 μ A; 78.5 k Ω ; 13 M Ω ; 27 mV




$$R_{in} = \frac{R_G}{1 + g_m R_D} = 0.5 \text{ M} \quad \left. \begin{array}{l} g_m R_D = 25 \\ \Rightarrow R_G = 13 \text{ M} \Omega \end{array} \right\}$$

$$\begin{aligned} I_D &= \frac{1}{2} k_n V_{OV}^2 \\ k_n V_{OV} &= \frac{25}{R_D} \\ V_{OV} &= 5 - R_D I_D - 0.7 \end{aligned} \quad \left. \begin{array}{l} \Rightarrow V_{OV} = 0.319 \text{ V} \\ \therefore I_D = 50.9 \mu\text{A} \\ R_D = 78.5 \text{ k} \Omega \end{array} \right\}$$

$$\hat{v}_{i, \max} = \frac{V_t}{|A_v| + 1} = \frac{0.7}{26} = 27 \text{ mV}$$

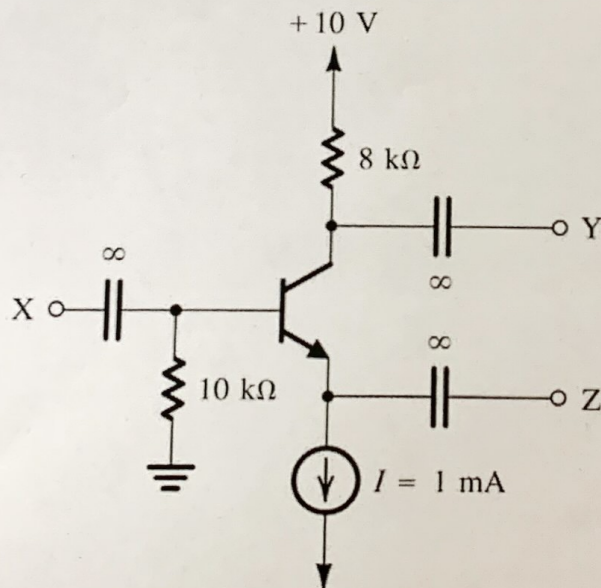7.20 The transistor in Fig. E7.20 is biased with a constant current source $I = 1$ mA and has $\beta = 100$ and $V_A = 100$ V.

- Neglecting the Early effect, find the dc voltages at the base, emitter, and collector.
- Find g_m , r_π , and r_o .
- If terminal Z is connected to ground, X to a signal source v_{sig} with a source resistance $R_{sig} = 2$ k Ω , and Y to an 8-k Ω load resistance, use the hybrid- π model shown in Fig. 7.26 to draw the small-signal equivalent circuit of the amplifier. (Note that the current source I should be replaced with an open circuit.) Calculate the overall voltage gain v_y/v_{sig} . If r_o is neglected, what is the error in estimating the gain magnitude? (Note: An infinite capacitance is used to indicate that the capacitance is large enough to act as a short circuit at all signal frequencies of interest. However, the capacitor still blocks dc.)



$$I_B = \frac{1 \text{ mA}}{100} = 10 \mu\text{A}$$

$$V_B = 0 - 10 \text{ k} \cdot 10 \mu = -0.1 \text{ V}$$


$$V_E = V_B - 0.7 = -0.8 \text{ V}$$

$$V_C = 10 - 8 \text{ k} \cdot 1 \text{ mA} = 2 \text{ V}$$

$$g_m = \frac{I_C}{V_T} = \frac{1}{25} \text{ S}$$

$$r_\pi = \frac{\beta}{g_m} = 2.5 \text{ k}\Omega$$

$$r_o = \frac{|V_A|}{I_C} = 100 \text{ k}\Omega$$

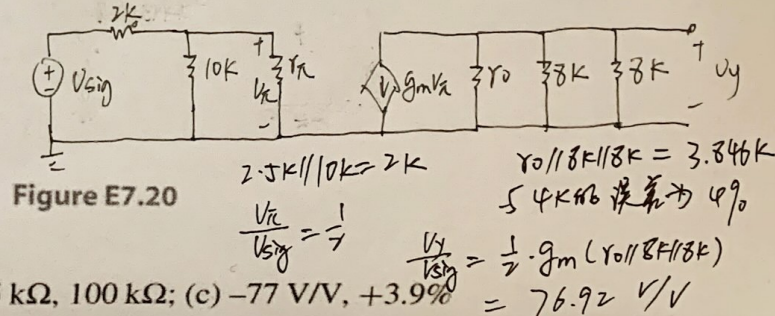

Ans. (a) -0.1 V, -0.8 V, $+2.1$ V; (b) 40 mA/V, 2.5 k Ω , 100 k Ω ; (c) -77 V/V, $+3.9\%$