

作业

D8.2 For the circuit of Fig. 8.4, let $V_{DD} = V_{SS} = 1.5$ V, $V_{tn} = 0.6$ V, $V_{tp} = -0.6$ V, all channel lengths = $1\text{ }\mu\text{m}$, $k'_n = 200\text{ }\mu\text{A/V}^2$, $k'_p = 80\text{ }\mu\text{A/V}^2$, and $\lambda = 0$. For $I_{REF} = 10\text{ }\mu\text{A}$, find the widths of all transistors to obtain $I_2 = 60\text{ }\mu\text{A}$, $I_3 = 20\text{ }\mu\text{A}$, and $I_5 = 80\text{ }\mu\text{A}$. It is further required that the voltage at the drain of Q_2 be allowed to go down to within 0.2 V of the negative supply and that the voltage at the drain of Q_5 be allowed to go up to within 0.2 V of the positive supply.

Ans. $W_1 = 2.5\text{ }\mu\text{m}$; $W_2 = 15\text{ }\mu\text{m}$; $W_3 = 5\text{ }\mu\text{m}$; $W_4 = 12.5\text{ }\mu\text{m}$; $W_5 = 50\text{ }\mu\text{m}$

对 Q_1 : $10\text{ }\mu\text{A} = \frac{1}{2} \cdot 200\text{ }\mu\text{A/V}^2 \cdot \frac{W_1}{1\text{ }\mu\text{m}} \cdot (0.2\text{ V})^2$

$\Rightarrow W_1 = 2.5\text{ }\mu\text{m}$

$\therefore \frac{W_2}{W_1} = \frac{60}{10} \Rightarrow W_2 = 15\text{ }\mu\text{m}$

$\frac{W_3}{W_1} = \frac{20}{10} \Rightarrow W_3 = 5\text{ }\mu\text{m}$

对 Q_4 :

$20\text{ }\mu\text{A} = \frac{1}{2} \cdot 80 \cdot \frac{W_4}{1} \cdot (0.2\text{ V})^2$

$\Rightarrow W_4 = 12.5\text{ }\mu\text{m}$

$\frac{W_5}{W_4} = \frac{80}{20} \Rightarrow W_5 = 50\text{ }\mu\text{m}$

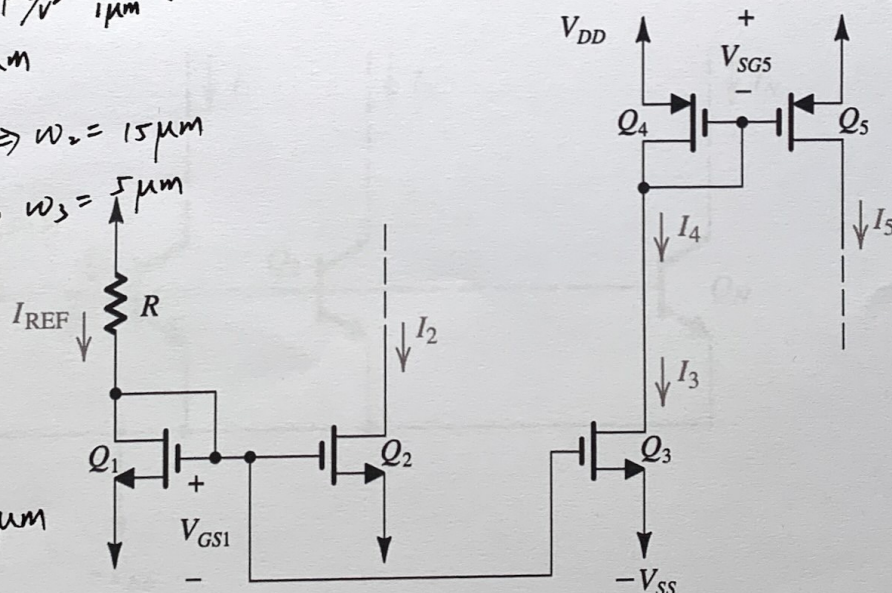



Figure 8.4 A current-steering circuit.

作业

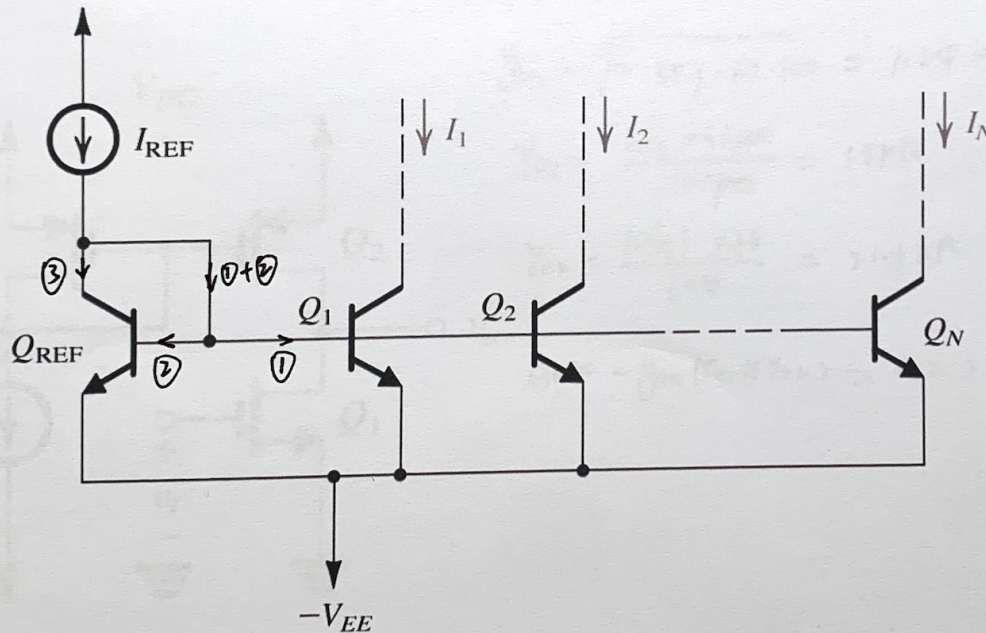8.5 Figure E8.5 shows an N -output current mirror. Assuming that all transistors are matched and have finite β and ignoring the effect of finite output resistances, show that

$$I_1 = I_2 = \dots = I_N = \frac{I_{REF}}{1 + (N+1)/\beta}$$

~~For $\beta = 100$, find the maximum number of outputs for an error not exceeding 10%.~~




$$\begin{aligned} \frac{I_i}{\beta} \cdot N + \frac{I_i}{\beta} + I_i &= I_{REF} \\ I_i \left(\frac{N}{\beta} + \frac{1}{\beta} + 1 \right) &= I_{REF} \\ I_i &= \frac{I_{REF}}{1 + (N+1)/\beta} \end{aligned}$$

Figure E8.5

8.8 A CMOS common-source amplifier such as that in Fig. 8.16(a), fabricated in a $0.18\text{-}\mu\text{m}$ technology, has $W/L = 7.2\text{ }\mu\text{m}/0.36\text{ }\mu\text{m}$ for all transistors, $k'_n = 387\text{ }\mu\text{A}/\text{V}^2$, $k'_p = 86\text{ }\mu\text{A}/\text{V}^2$, $I_{\text{REF}} = 100\text{ }\mu\text{A}$, $V'_{An} = 5\text{ V}/\mu\text{m}$, and $|V'_{Ap}| = 6\text{ V}/\mu\text{m}$. Find g_{m1} , r_{o1} , r_{o2} , and the voltage gain.

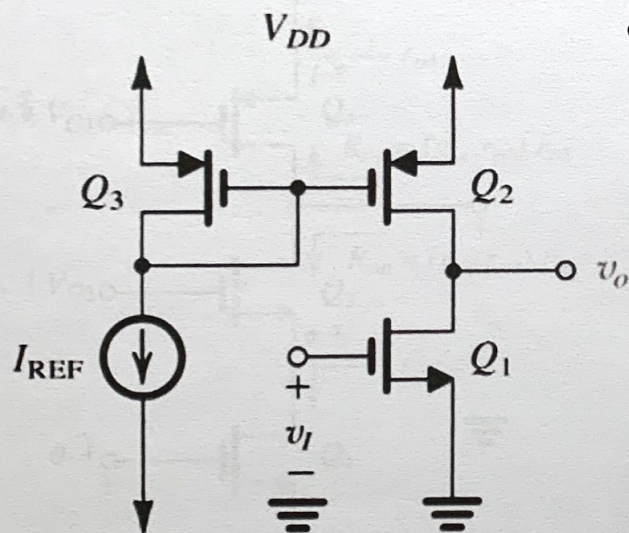Ans. $1.24\text{ mA}/\text{V}$; $18\text{ k}\Omega$; $21.6\text{ k}\Omega$; $-12.2\text{ V}/\text{V}$



(a)

$$I_{D1} = I_{\text{REF}} = 100\text{ }\mu\text{A}$$

$$g_{m1} = \sqrt{2 \cdot 387 \cdot 20 \cdot 100} = 1.24\text{ mA}/\text{V}$$


$$r_{o1} = \frac{V'_{An} \cdot 0.36\text{ }\mu\text{m}}{100\text{ }\mu\text{A}} = 18\text{ k}\Omega$$

$$r_{o2} = \frac{|V'_{Ap}| \cdot 0.36}{100} = 21.6\text{ k}\Omega$$

$$A_v = -g_{m1}(r_{o1} \parallel r_{o2}) = -12.2\text{ V}/\text{V}$$

- 8.20 Consider the cascode amplifier of Fig. 8.31 with the dc component at the input, $V_i = 0.7$ V, $V_{G2} = 1.0$ V, $V_{G3} = 0.8$ V, $V_{G4} = 1.1$ V, and $V_{DD} = 1.8$ V. If all devices are matched (i.e., if $k_{n1} = k_{n2} = k_{p3} = k_{p4}$), and have equal $|V_t|$ of 0.5 V, what is the overdrive voltage at which the four transistors are operating? What is the allowable voltage range at the output?

Ans. 0.2 V; 0.5 V to 1.3 V

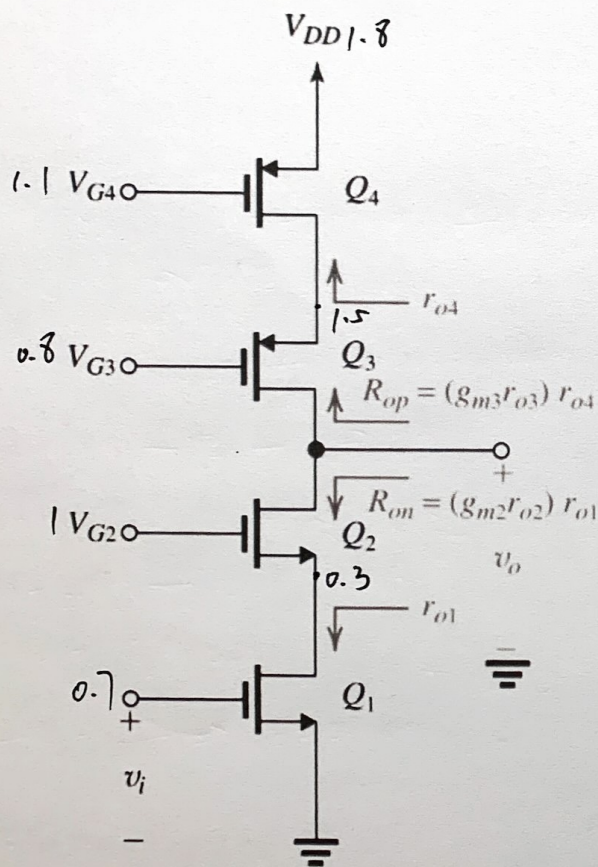

(a)

$$V_{OV} = 0.7 - 0.5 = 0.2 \text{ V}$$

根据图, V_{out} 的上限是 $1.5 - 0.2 = 1.3$

$$V_{out} \text{ 的下限是 } 0.3 + 0.2 = 0.5$$