

例9

1.	$Q_2 Q_1 Q_0$	Z	X	$Q_2^* Q_1^* Q_0^*$	SET
	0 0 0	1	X	0 0 0	0
	0 0 0	0	X	0 0 1	0
	0 0 1	1	X	0 1 1	0
	0 0 1	0	X	0 1 0	0
	0 1 0	X	0	0 1 0	0
	0 1 0	X	1	0 0 0	0
	0 1 1	X	X	1 0 0	0
	1 0 0	X	0	1 0 0	0
	1 0 0	X	1	0 0 0	1

状态方程 $Q_0^* = \bar{Q}_2 \bar{Q}_1 \bar{Q}_0 \bar{Z} + \bar{Q}_2 \bar{Q}_1 Q_0 Z$

$Q_1^* = \bar{Q}_2 \bar{Q}_1 Q_0 + \bar{Q}_2 Q_1 \bar{Q}_0 X$

$Q_2^* = \bar{Q}_2 Q_1 Q_0 + Q_2 \bar{Q}_1 \bar{Q}_0 X$

输出方程 $SET = Q_2 X$ (考虑无关项)

驱动方程 $D_0 = \bar{Q}_2 \bar{Q}_1 \bar{Q}_0 \bar{Z} + \bar{Q}_2 Q_1 Q_0 Z$

$D_1 = \bar{Q}_2 \bar{Q}_1 Q_0 + \bar{Q}_2 Q_1 \bar{Q}_0 X$

$D_2 = \bar{Q}_2 Q_1 Q_0 + Q_2 \bar{Q}_1 \bar{Q}_0 X$



C 2.

Q_1	Q_0	$A > B$	Q_1^*	Q_0^*	LDRA	LDRB	CAP
0	0	*	0	1	0	1	0
0	1	*	1	0	1	0	0
1	0	*	1	1	0	1	0
1	1	1	1	0	0	0	1
1	1	0	0	1	0	0	1

Q_0^*
 $Q_0^* = Q_1 \overline{(A > B)} + \overline{Q_0}$
 $Q_1^* = \overline{Q_1} Q_0 + Q_1 \overline{Q_0} + (A > B) Q_0$
 $LDRA = \overline{Q_1} Q_0$
 $LDRB = \overline{Q_0}$
 $CAP = Q_1 Q_0$

Q_1^*
 $Q_1^* = \overline{Q_1} Q_0 + Q_1 \overline{Q_0} + (A > B) Q_0$
 $LDRA = \overline{Q_1} Q_0$
 $LDRB = \overline{Q_0}$
 $CAP = Q_1 Q_0$

3.

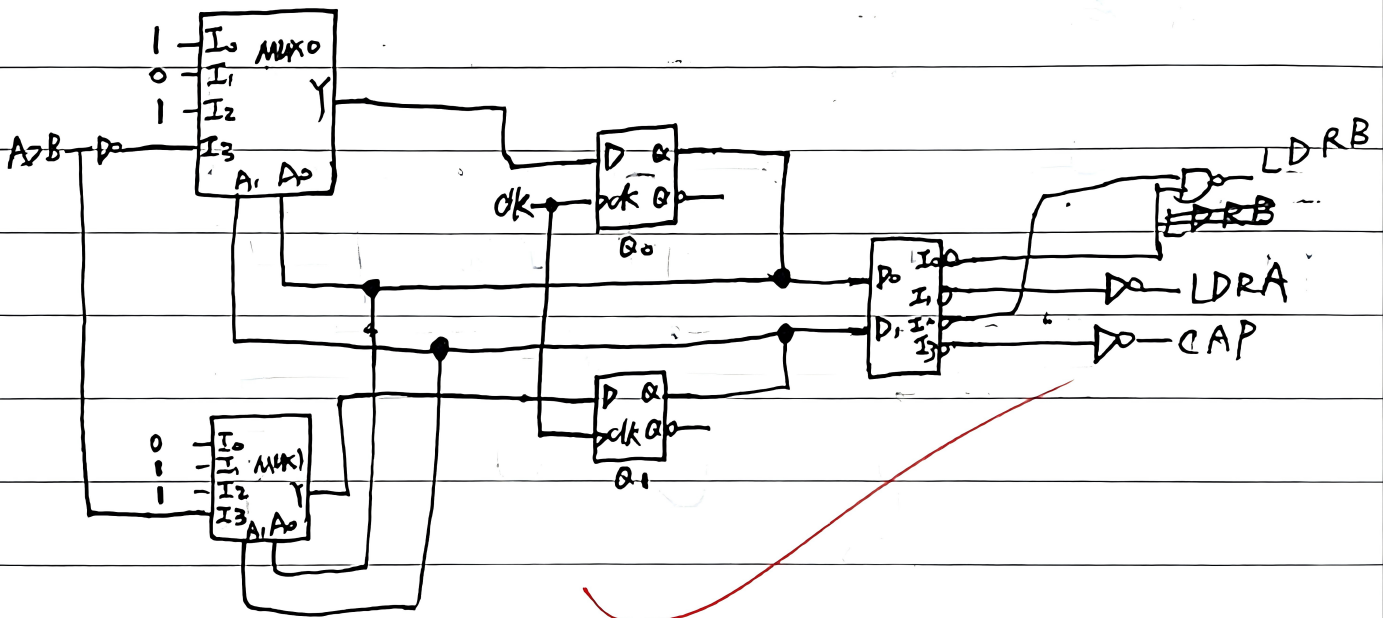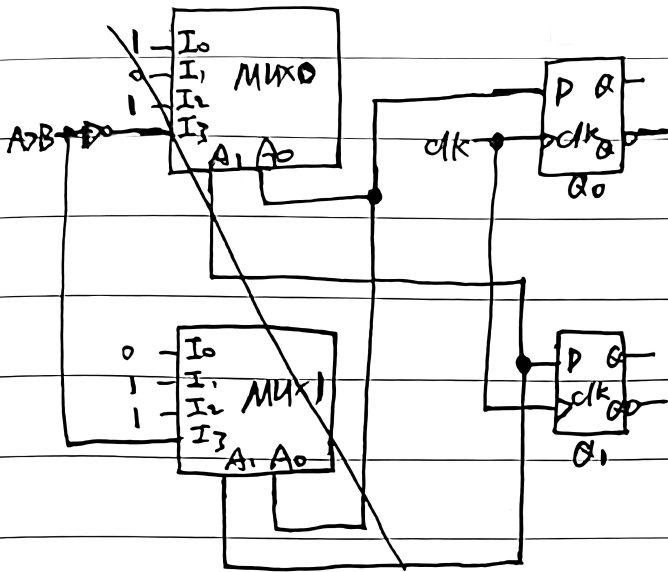

8.

者

$$LDRA = \theta_b T_2$$

$$LDRB = (Q_a + Q_c) T_2$$

$$CAP = Q \alpha T_2$$

T₂ 操作寄存器电平控制信号

