
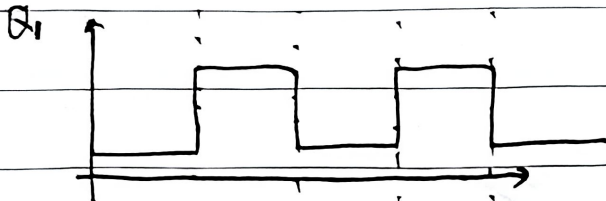




作业 6

5.21, 22, 23, 24, 25, 30, 35, 37


5.21 CLK 低电平触发 下降沿触发

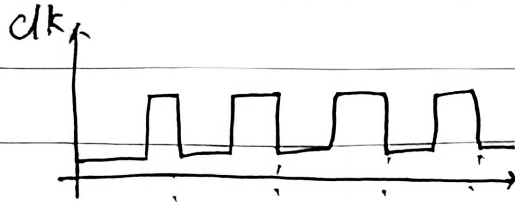

$$f_1 = \frac{1}{2} f_{clk}$$

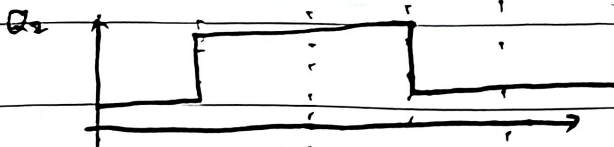
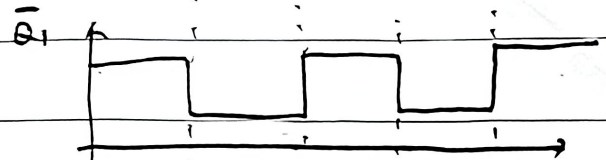


$$f_2 = \frac{1}{4} f_{clk}$$

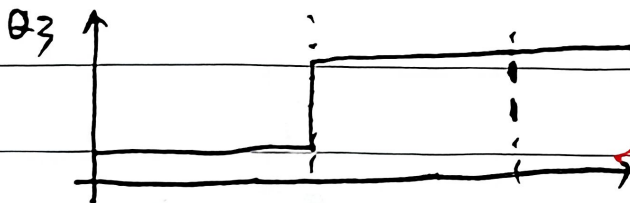


$$f_3 = \frac{1}{8} f_{clk}$$


22

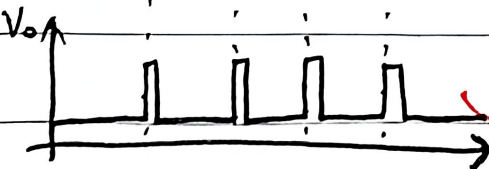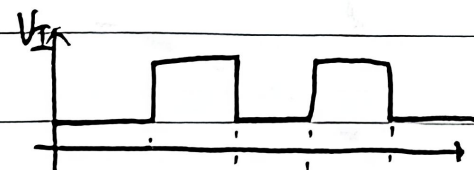


5.23

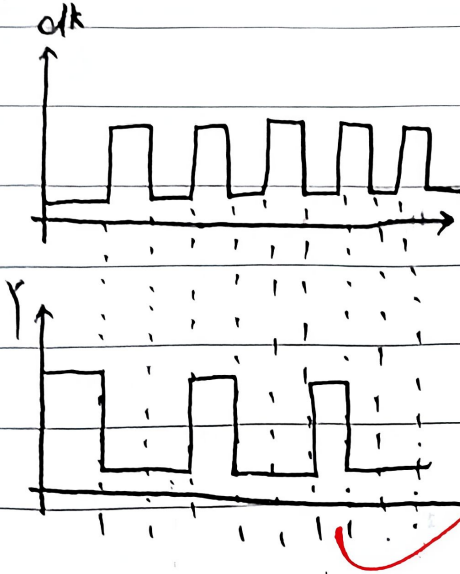

5.24

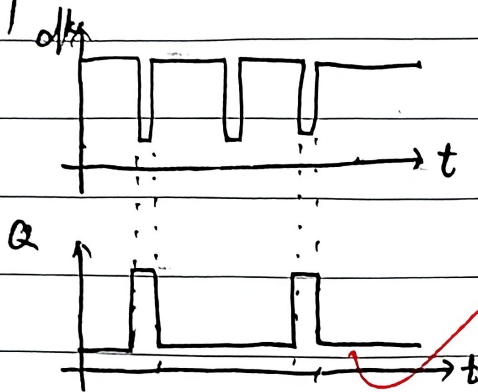

5.25

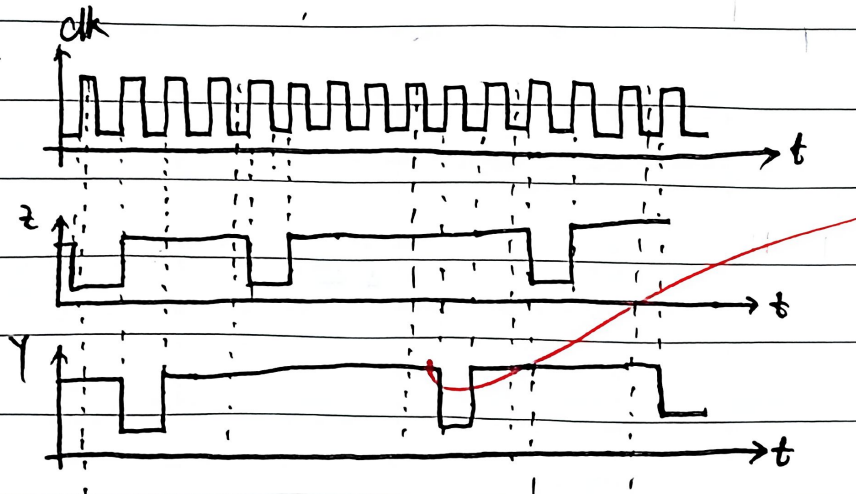


~~A9 A8 A7 A6 A5 A4~~

5.30

将 A_i 地址线、~~R/W 线~~ 与 R/W 线与 CS 线分别


并联即可 每 I/O 端作 整个 ROM 输入/输出一位

5.35

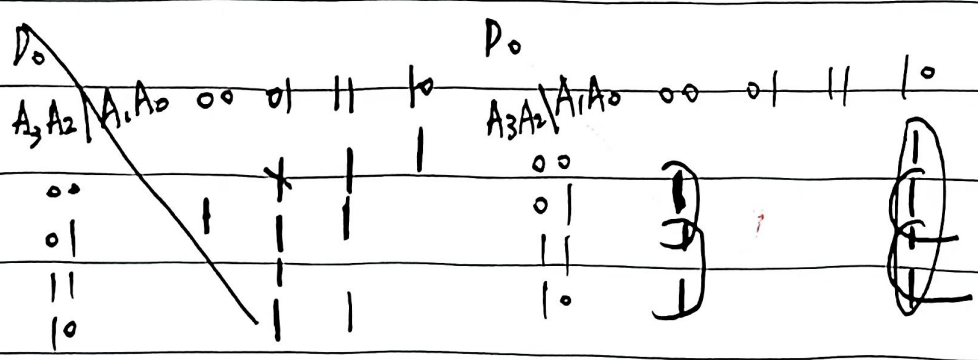


$$D_0 = A_1 \bar{A}_0 + A_2 \bar{A}_0 + A_3 \bar{A}_0$$

D_1

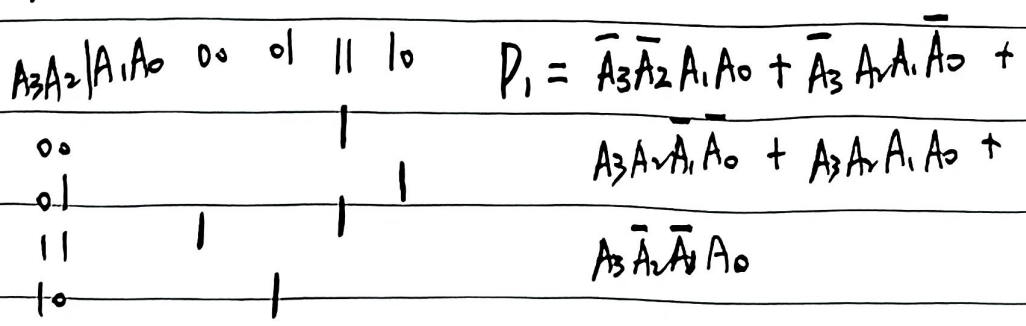

$$D_1 = \bar{A}_3 \bar{A}_2 A_1 A_0 + \bar{A}_3 A_2 A_1 \bar{A}_0 + A_3 \bar{A}_2 \bar{A}_1 \bar{A}_0 + A_3 A_2 A_1 A_0 + A_3 \bar{A}_2 \bar{A}_1 A_0$$

D_2

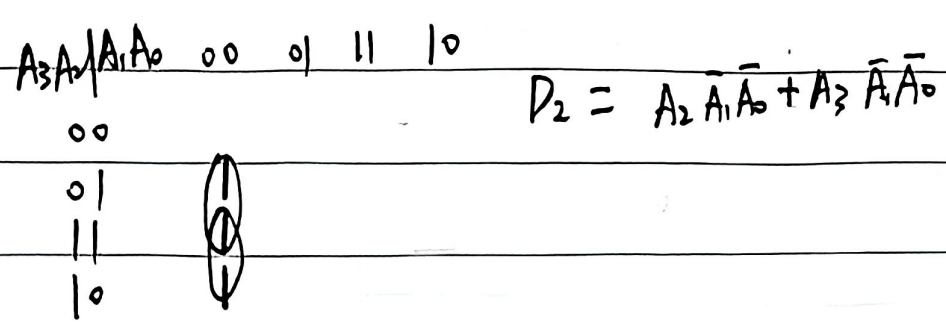

$$D_2 = A_2 \bar{A}_1 \bar{A}_0 + A_3 \bar{A}_1 \bar{A}_0$$

D₃


A ₃ A ₂	A ₁ A ₀	00	01	11	10
00	01	1			
01	11		1		
10	11			1	
11	10				1

$$D_3 = \bar{A}_3 \bar{A}_2 \bar{A}_1 \bar{A}_0 + \bar{A}_3 A_2 \bar{A}_1 A_0 + A_3 A_2 A_1 A_0 + A_3 A_2 \bar{A}_1 \bar{A}_0$$

5.37

2⁴ × 4 ROM

~~地址 A₃A₂A₁~~

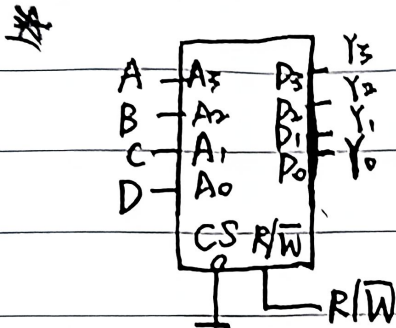

A ₃	A ₂	A ₁	A ₀	D ₃	D ₂	D ₁	D ₀
0	0	0	0	1	0	0	1
0	0	0	1	0	0	0	0
0	0	1	0	0	0	0	1
0	0	1	1	0	1	0	0
0	1	0	0	0	0	0	1
0	1	0	1	0	0	1	0
0	1	1	0	0	0	0	1
0	1	1	1	0	1	0	0
1	0	0	0	0	1	0	0
1	0	0	1	0	0	0	0
1	0	1	0	0	0	1	0
1	0	1	1	1	0	0	0
1	1	0	0	0	1	0	0
1	1	0	1	0	0	1	0
1	1	1	0	0	1	0	0
1	1	1	1	0	0	0	0

98